# Combinatorial Logic Project 2 Lab 3 - RBN - 2306173113 - Athazahra Nabila Ruby - KKI

Design Procedure

### 1. Specification

- BCD to Excess-5 converter
- Transforms BCD code for the decimal digits to Excess-5 for the decimal digits
- BCD code words for digits 0 through 9: 4-bit patterns 0000 to 1001, respectively
- Excess-5 code words for digits 0 through 9: 4-bit patterns consisting of 5 (binary 0101) added to each BCD code word
- Implementation:
  - NOR gates

# 2. Formulation

#### Variables:


BCD (input): A, B, C, DExcess-5 (output): W, X, Y, Z


Don't Cares: BCD 1010 to 1111


## **Truth Table**


BCD				Excess-5			
Α	В	С	D	W	Х	Υ	Z
0	0	0	0	0	1	0	1
0	0	0	1	0	1	1	0
0	0	1	0	0	1	1	1
0	0	1	1	1	0	0	0
0	1	0	0	1	0	0	1
0	1	0	1	1	0	1	0
0	1	1	0	1	0	1	1
0	1	1	1	1	1	0	0
1	0	0	0	1	1	0	1
1	0	0	1	1	1	1	0
1	0	1	0	Х	Х	Х	Х
1	0	1	1	Х	Х	Х	X
1	1	0	0	Х	Х	Х	X
1	1	0	1	Χ	Х	Х	Х
1	1	1	0	Χ	Х	Х	Х
1	1	1	1	Х	Х	Х	Х

### 3. Optimization

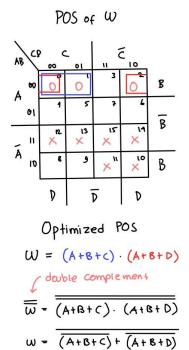

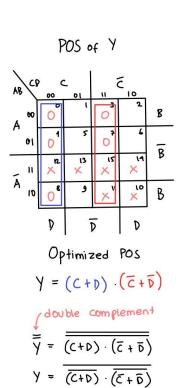

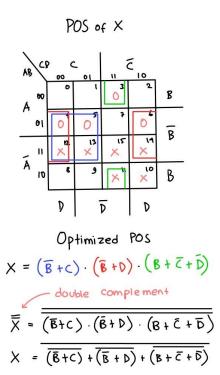

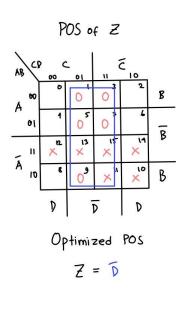

Note: double complement is used to make converting into NOR gates easier.

# 4. Technology Mapping

