

Lab 7 - Register

Athazahra Nabila Ruby - RBN - KK1 - 2306173113

1) State table

Control Input		Present State	Input	next State
S_1	S_0	$A_i(t)$	$B_i(t)$	$A_i(t+1)$
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	0
1	1	1	1	0


2) optimization

		$A_i \bar{B}_i$		\bar{A}_i		A_i		
S_1	S_0	00	01	11	10			\bar{S}_0
	\bar{S}_1	0	1	3	2			
S_1	S_0	1	5	7	6			S_0
	\bar{S}_1	12	13	15	14			
		8	9	10	10			S_0
		\bar{B}_1	B_1	\bar{B}_1	B_1			

$$\begin{aligned}
 A_i(t+1) &= S_1 \bar{S}_0 A_i + S_1 \bar{S}_0 B_i + S_1 S_0 \bar{A}_i + S_0 \bar{A}_i B_i + \bar{S}_0 A_i B_i + \bar{S}_1 \bar{S}_0 \bar{A}_i \bar{B}_1 \\
 &= S_1 (\bar{S}_0 A_i + S_0 \bar{A}_i) + B_i (S_0 \bar{A}_i + \bar{S}_0 A_i) + (\bar{S}_1 \bar{B}_1) (\bar{S}_0 \bar{A}_i) + S_1 \bar{S}_0 B_i \\
 &= S_1 (S_0 \oplus A_i) + B_i (S_0 \oplus A_i) + (\bar{S}_1 + B_1) (\bar{S}_0 \bar{A}_i) + S_1 \bar{S}_0 B_i \\
 &= (S_1 + B_i) (S_0 \oplus A_i) + (\bar{S}_1 + B_1) (\bar{S}_0 \bar{A}_i) + S_1 \bar{S}_0 B_i
 \end{aligned}$$


•) Combinational (without Mux)
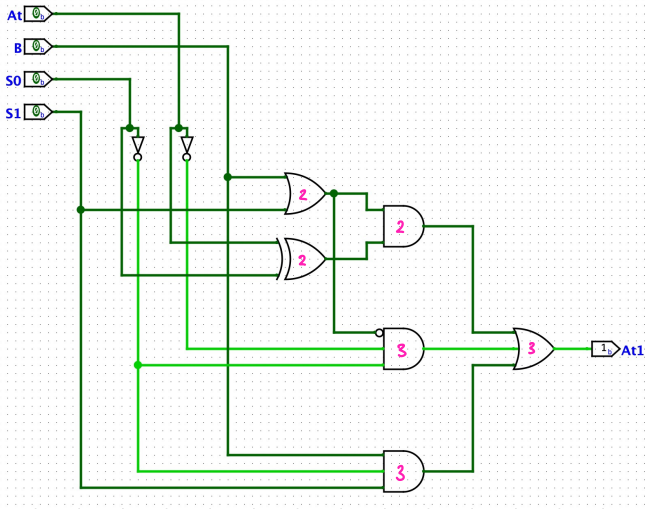
$$\text{Gate cost} = 2 + 2 + 2 + 3 + 3 + 3 = 15$$




•) Combinational with Mux
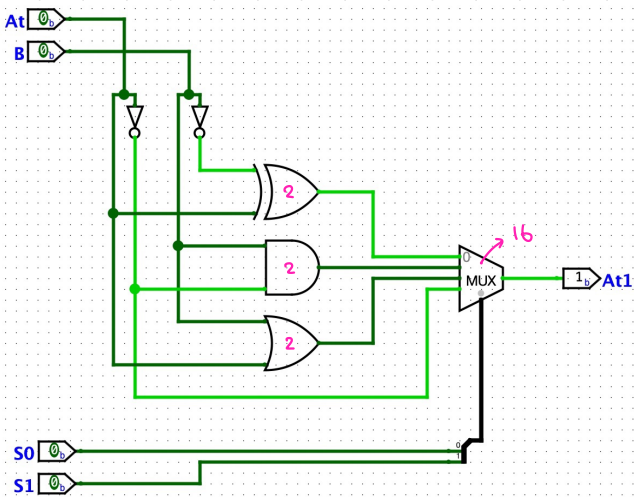
$$\text{Gate cost} = 2 + 2 + 2 + 16 = 22$$




•) 4-bit register without Mux

$$\text{Gate Cost} = 15 \times 4 = 60$$

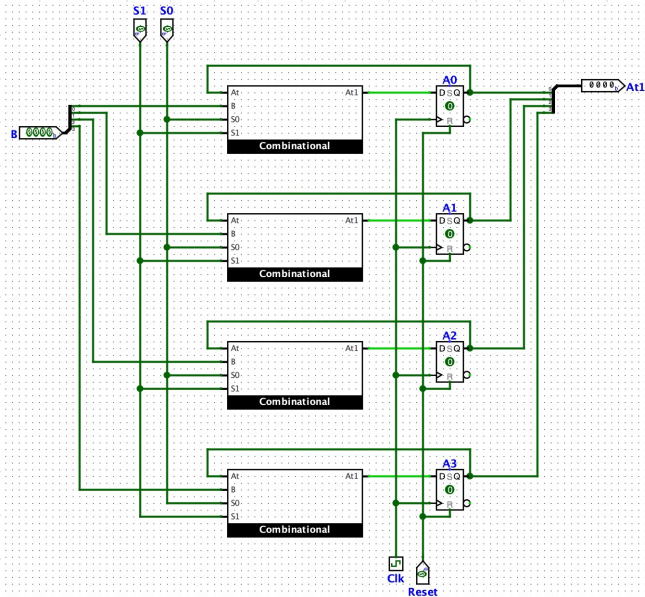

•) 4-bit register with MUX

$$\text{Gate Cost} = 22 \times 4 = 88$$

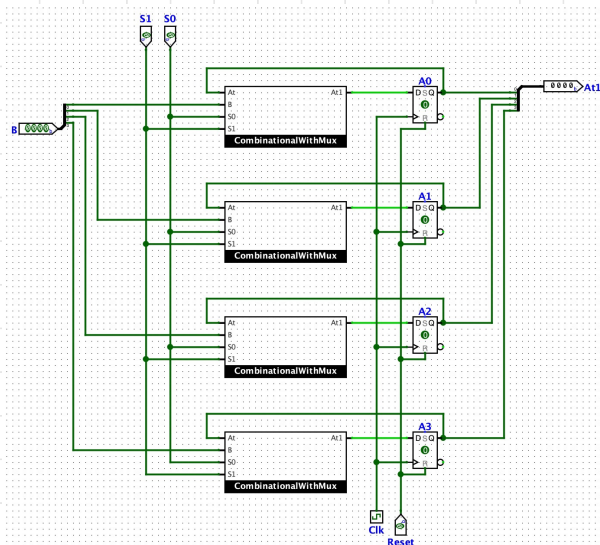

•) Answer to Trivia : Based on the gate cost calculations above, we can conclude that the circuit that uses MUX has a larger gate cost than the circuit that does not use MUX. Therefore, it is more expensive to make a circuit that uses a MUX as opposed to no MUX.